

SOLUTIONS

EECS 281: Homework #1


Due: Tuesday, January 18, 2004

Name: _____

Email: _____

1. Given the boolean expression: $f(a, b) = (a + b)(\overline{a \cdot b})$

(a) Draw the logic gate schematic:

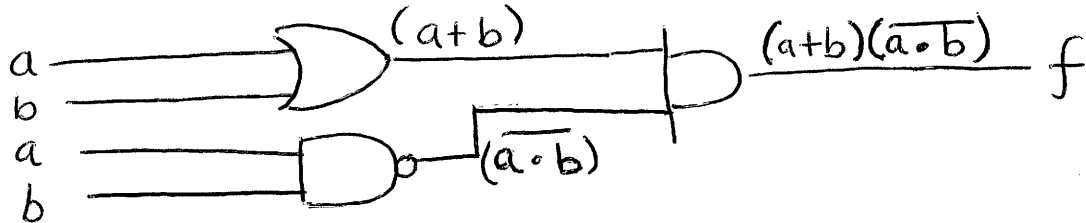

(b) Re-write as a C++/JAVA expression: $f = (a | b) \& \sim (a \& b);$ **bitwise**

(c) Re-write as a VHDL expression: $f <= (a \text{ OR } b) \text{ AND } (a \text{ NAND } b);$


(d) Fill in the truth table

a	b	$a + b$	$a \cdot b$	$\overline{a \cdot b}$	$f = (a + b)(\overline{a \cdot b})$
0	0	0	0	1	0
0	1	1	0	1	1
1	0	1	0	1	1
1	1	1	1	0	0

logical c++/Java expression

$$f = (a || b) \&\& !(a \&\& b);$$

2. Given the following logic circuit

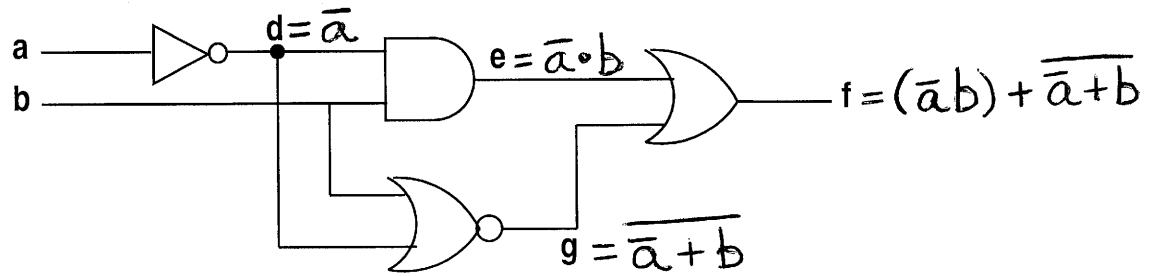

(a) Give the truth table of a, b, c, d, e, g and f:

a	b	$d = \bar{a}$	$e = \bar{a}b$	$g = \overline{\bar{a} + b}$	$f = \bar{a}b + \overline{\bar{a} + b}$
0	0	1	0	0	0
0	1	1	1	0	1
1	0	0	0	1	1
1	1	0	0	0	0

(b) Give the boolean expression of e, g and f:

$$e = \bar{a}b$$

$$g = \overline{\bar{a} + b}$$


$$f = \bar{a}b + \overline{\bar{a} + b}$$

(c) Compare the truth table of part 1d with 2a. Are they the same? Yes or No. Yes

What other common logic function is $f(a, b)$ similar to?


XOR

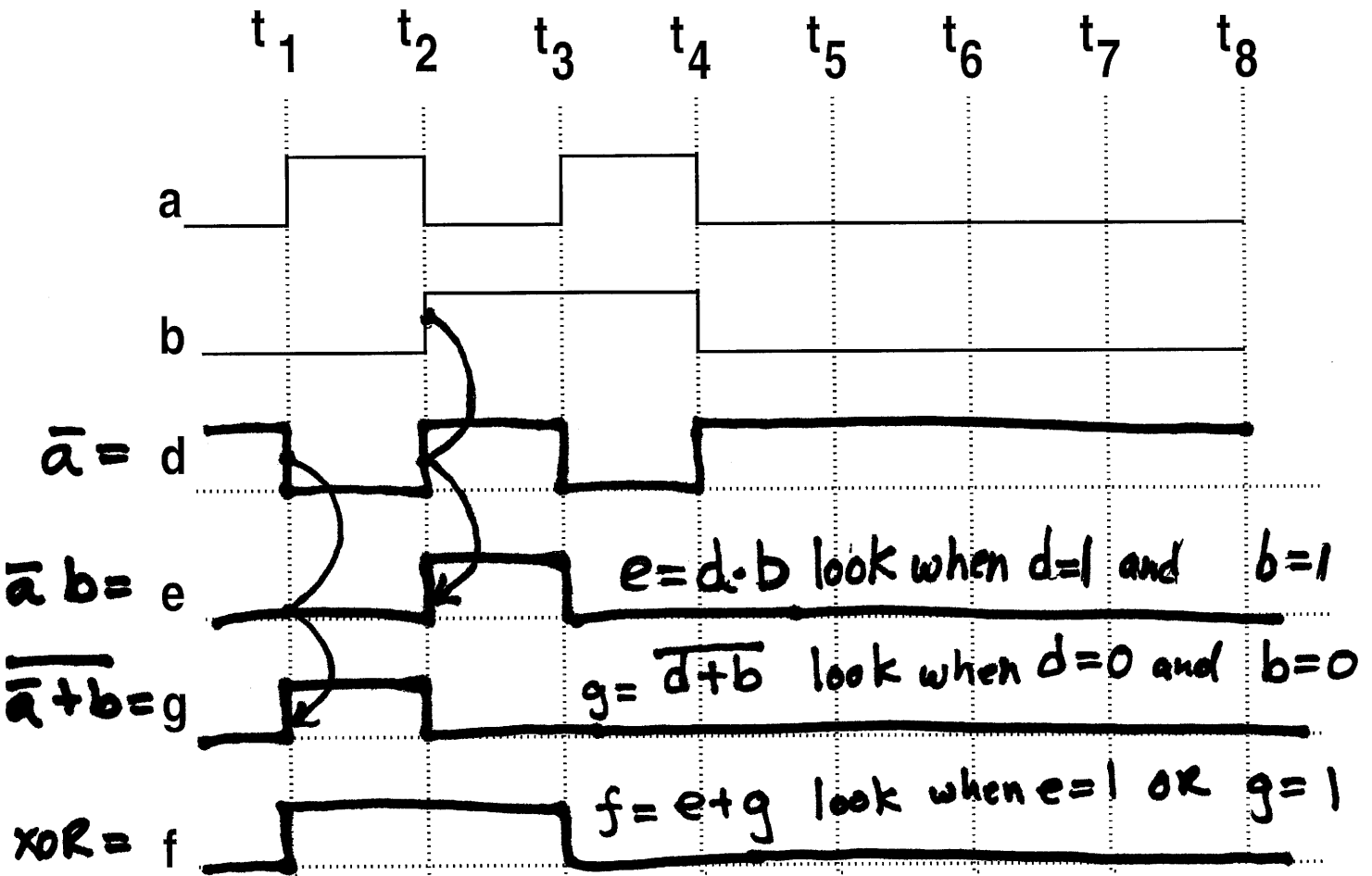(d) Fill in the timing diagram including trigger lines (0 ns delay) for 2(a).



	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8
a	0	1	0	1	0	0	0	0	
b	0	0	1	1	0	0	0	0	
d	1	0	1	0	1	1	1	1	
e	0	0	1	0	0	0	0	0	
g	0	1	0	0	0	0	0	0	
f	0	1	1	0	0	0	0	0	

3. Given the following logic circuit

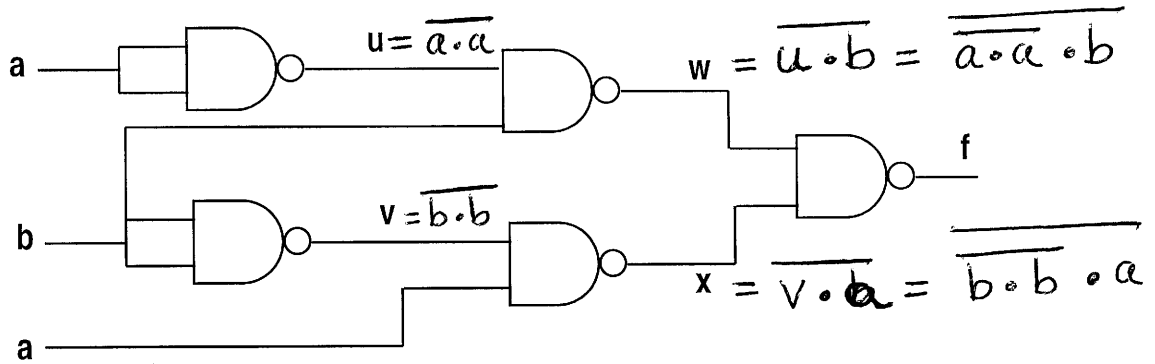

(a) Give the truth table of a, b, u, v, w, x and f:

a	b	$u = \overline{a \cdot a} = \bar{a}$	$v = \overline{b \cdot b} = \bar{b}$	$w = \overline{u \cdot b}$	$x = \overline{v \cdot a}$	$f = \overline{w \cdot x}$
0	0	1	1	1	1	0
0	1	1	0	0	1	1
1	0	0	1	1	0	1
1	1	0	0	1	1	0

(b) Give the boolean expression of $f(a, b) =$ _____

(c) Re-write as a C++/JAVA expression: $f =$ _____

$\sim (\sim (\sim (a \# a) \# b) \# \sim (\sim (b \# b) \# a)) ;$

(d) Re-write as a VHDL expression: $f <=$ _____

$((a \text{ NAND } a) \text{ NAND } b) \text{ NAND } ((b \text{ NAND } b) \text{ NAND } a);$

$u = \overline{a \cdot a}$

$v = \overline{b \cdot b}$

$w = \overline{u \cdot b} = \overline{\overline{a \cdot a} \cdot b}$

$x = \overline{v \cdot a} = \overline{\overline{b \cdot b} \cdot a}$

$f = \overline{w \cdot x} = \overline{(\overline{\overline{a \cdot a} \cdot b}) (\overline{\overline{b \cdot b} \cdot a})}$