



EECS 318 CAD Computer Aided Design

LECTURE 4: Delay models & std_ulogic

*Instructor: Francis G. Wolff
wolff@eecs.cwru.edu*

Case Western Reserve University

This presentation uses powerpoint animation: please viewshow

Delta Delay

- **Default signal assignment propagation delay if no delay is explicitly prescribed**
 - **VHDL signal assignments do not take place immediately**
 - **Delta is an infinitesimal VHDL time unit so that all signal assignments can result in signals assuming their values at a future time**

- **E.g.**


```
Output <= NOT Input;  
-- Output assumes new value in one delta cycle
```

- **Supports a model of concurrent VHDL process execution**
 - **Order in which processes are executed by simulator does not affect simulation output**

Delta Delay

An Example with Delta Delay

- What is the behavior of C?

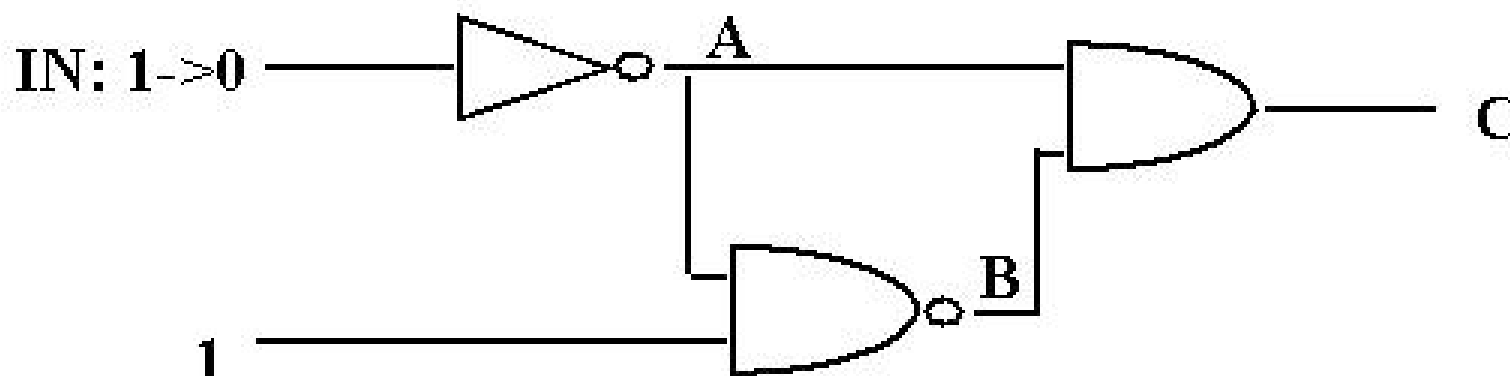

Using delta delay scheduling

Time	Delta	Event
0 ns	1	IN: 1->0 eval INVERTER
	2	A: 0->1 eval NAND, AND
	3	B: 1->0 C: 0->1 eval AND
	4	C: 1->0
1 ns		

Inertial Delay


- Provides for specification propagation delay and input pulse width, i.e. 'inertia' of output:

```
target <= [REJECT time_expression] INERTIAL waveform;
```

- Inertial delay is default and REJECT is optional :

```
Output <= NOT Input AFTER 10 ns;  

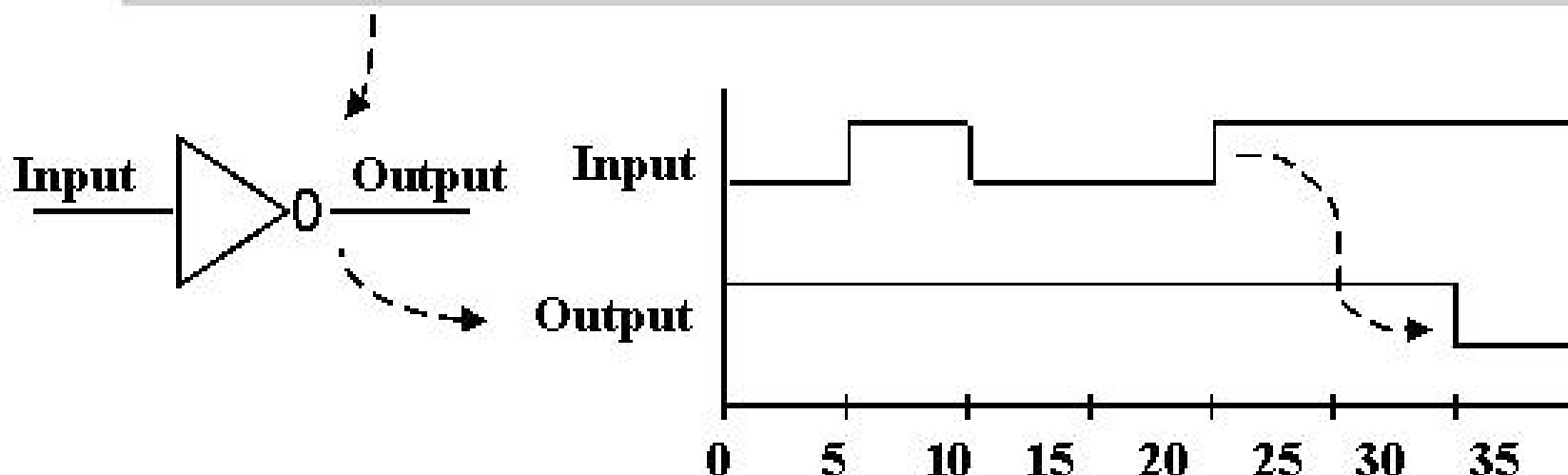
-- Propagation delay and minimum pulse width are 10ns
```




Transport Delay

- Transport delay must be explicitly specified
 - I.e. keyword “TRANSPORT” must be used
- Signal will assume its new value after specified delay
 
```
-- TRANSPORT delay example  
Output <= TRANSPORT NOT Input AFTER 10 ns;
```



Inertial and Transport Delay

 

Combinatorial Logic Operators




#Transistors

2	NOT	$z \leq \text{NOT } (x); \quad z \leq \text{NOT } x;$
$2+2i$	AND	$z \leq x \text{ AND } y;$
$2i$	NAND	$z \leq \text{NOT } (x \text{ AND } y);$
$2+2i$	OR	$z \leq x \text{ OR } y;$
$2i$	NOR	$z \leq \text{NOT } (x \text{ OR } y);$
10	XOR	$z \leq (x \text{ and NOT } y) \text{ OR } (\text{NOT } x \text{ AND } y);$ $z \leq (x \text{ AND } y) \text{ NOR } (x \text{ NOR } y); \text{ --AOI}$
10	XNOR	$z \leq (x \text{ and } y) \text{ OR } (\text{NOT } x \text{ AND NOT } y);$ $z \leq (x \text{ NAND } y) \text{ NAND } (x \text{ OR } y); \text{ --OAI}$

Footnote: (i =#inputs) We are only referring to CMOS static transistor ASIC gate designs

Exotic XOR designs can be done in 6 (J. W. Wang, IEEE J. Solid State Circuits, 29, July 1994)

Std_logic AND: Un-initialized value

 

NOT	0	1	U
	1	0	U

AND	0	1	U
0	0	0	0
1	0	1	U
U	0	U	U

0 AND <anything> is 0


0 NAND <anything> is 1

OR	0	1	U
0	0	1	U
1	1	1	1
U	U	1	U

1 OR <anything> is 1

1 NOR <anything> is 0

Std_logic AND: X Forcing Unknown Value

 

NOT	0	X	1	U
	1	X	0	U

AND	0	X	1	U
0	0	0	0	0
X	0	X	X	U
1	0	X	1	U
U	0	U	U	U

0 AND <anything> is 0

0 NAND <anything> is 1

OR	0	X	1	U
0	0	X	1	U
X	X	X	1	U
1	1	1	1	1
U	U	U	1	U

1 OR <anything> is 1

0 NOR <anything> is 1

Modeling logic gate values: std_ulogic



TYPE **std_ulogic** IS (-- Unresolved LOGIC

 'Z', -- High Impedance (Tri-State)

 '1', -- Forcing 1

 'H', -- Weak 1

 'X', -- Forcing Unknown: i.e. combining 0 and 1

 'W', -- Weak Unknown: i.e. combining H and L

 'L', -- Weak 0


 '0', -- Forcing 0

 'U', -- Un-initialized

 '-' , -- Don't care

);


**Example:
multiple drivers**

 

The rising transition signal




$V_{CC}=5.5$ 25°C

 

Unknown
2.20 Volt
gap

 Multiple output drivers: Resolution Function



	U	X	0	L	Z	W	H	1	-
U	U	U	U	U	U	U	U	U	U
X	U	X	X	X	X	X	X	X	X
0	U	X	0	0	0	0	0	X	X
L									
Z									
W									
H									
1									
-	U	X	X	X	X	X	X	X	X

Suppose that
the first gate outputs a **1**
the second gate outputs a **0**
then
the mult-driver output is **X**
X: forcing unknown value by combining 1 and 0 together

Multiple output drivers: Resolution Function


	U	X	0	L	Z	W	H	1	-
U	U	U	U	U	U	U	U	U	U
X		X	X	X	X	X	X	X	X
0			0	0	0	0	0	X	X
L				L	L	W	W	1	X
Z					Z	W	H	1	X
W						W	W	1	X
H							H	1	X
1								1	X
-									X

Observe that 0 pulls down all weak signals to 0


H <driving> L => W

- Note the multi-driver resolution table is symmetrical

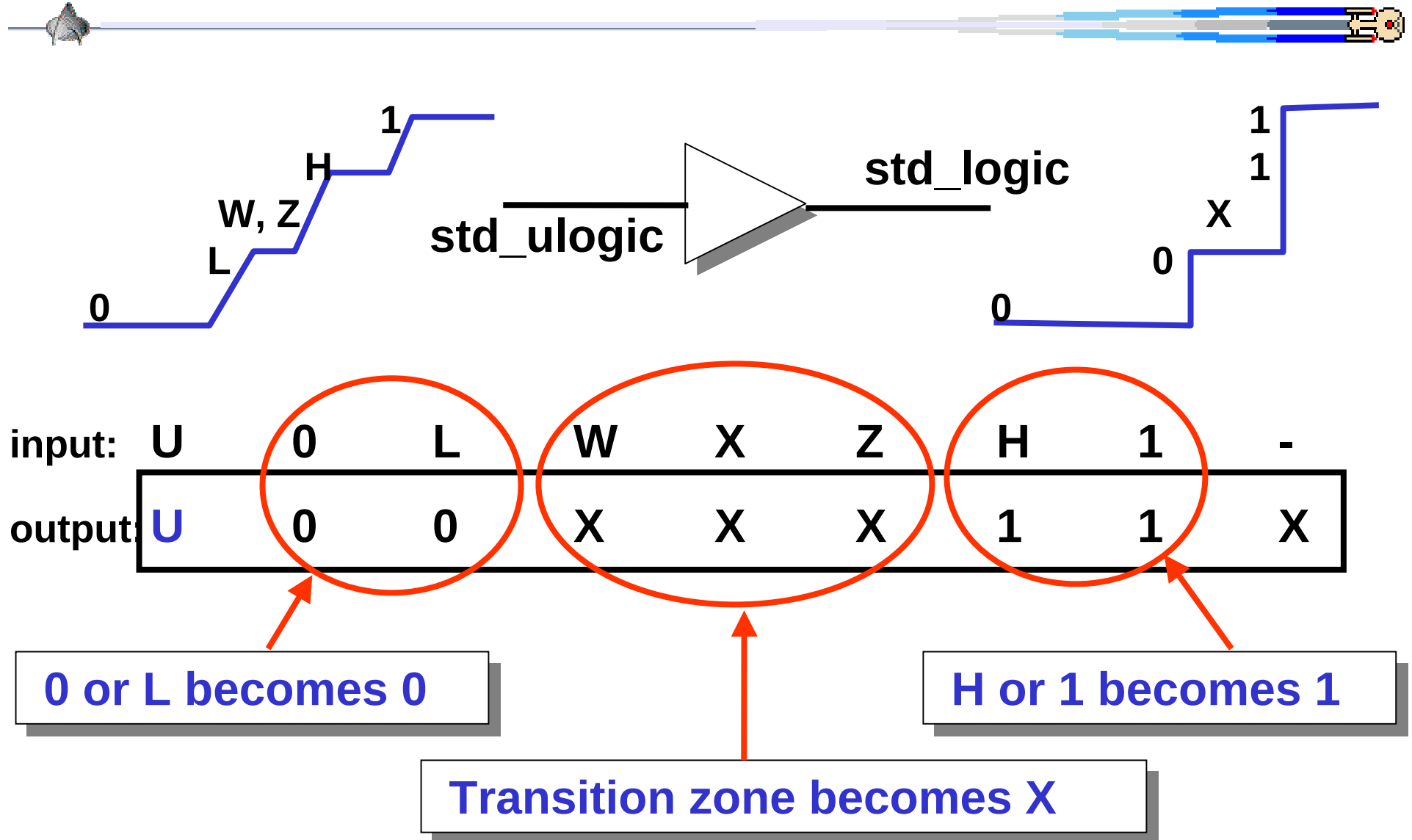Resolution Function: std_logic buffer gate



Resolving input: std_logic AND GATE

 

Process each input as an unresolved to resolved buffer.

Then process the gate as a standard logic gate { 0, X, 1, U }


For example, let's transform **z <= 'W' AND '1';**

z <= **'W'** AND '1'; -- convert std_ulogic **'W'** to std_logic **'X'**

z <= **'X'** AND '1'; -- now compute the std_logic AND

z <= **'X'**;


2-to-1 Multiplexor: with-select-when

 

structural

```
Y <= sa OR sb;  
sa <= a AND NOT s;  
sb <= b AND s;
```

combinatorial logic

 

behavioral

Only
values
allowed

```
WITH s SELECT  
  Y <= a WHEN '0',  
    b WHEN '1';
```

or alternatively

```
WITH s SELECT  
  Y <= a WHEN '0',  
    b WHEN OTHERS;
```


4-to-1 Multiplexor: with-select-when



```
Y <= sa OR sb OR sc OR sd;  
sa <= a AND ( NOT s(1) AND NOT s(0) );  
sb <= b AND ( NOT s(1) AND s(0) );  
sc <= c AND ( s(1) AND NOT s(0) );  
sd <= d AND ( s(1) AND s(0) );
```

Structural Combinatorial logic

 As the complexity of the combinatorial logic **grows**, the SELECT statement, **simplifies** logic design but at a **loss** of structural information




WITH **s** SELECT

```
Y <= a WHEN "00",  
     b WHEN "01",  
     c WHEN "10",  
     d WHEN OTHERS;
```

behavioral

Tri-State buffer

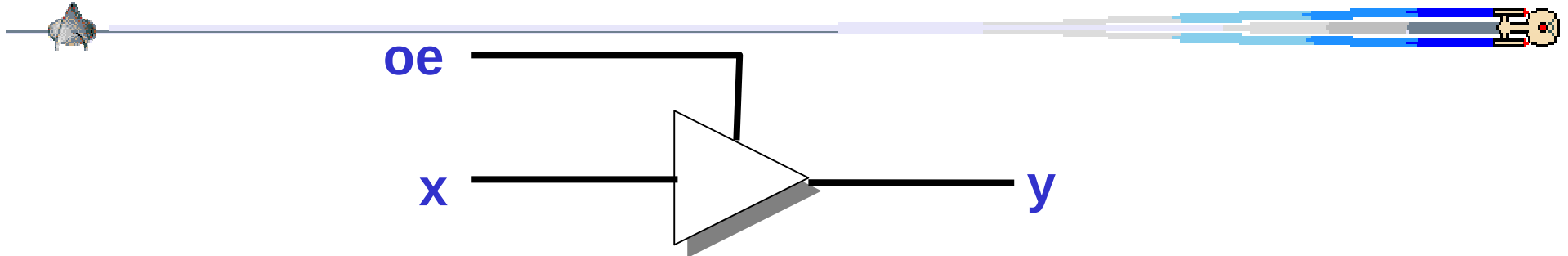

```
ENTITY Buffer_Tri_State IS
    PORT(x:      IN      std_logic;
          y:      OUT     std_logic;
          oe:     IN      std_logic
    ); END;
```


```
ARCHITECTURE Buffer3 OF Buffer_Tri_State IS
BEGIN
```

```
    WITH oe SELECT
```

```
    y <=  x WHEN '1', -- Enabled: y <= x;
          'Z' WHEN '0'; -- Disabled: output a tri-state
```


```
END;
```

 Assignment #2 (Part 1 of 3) Due Thurs, 9/14



- 1) Assume each gate is 10 ns delay for the above circuit.
 - (a) Write entity-architecture for a inertial model
 - (b) Given the following waveform, draw, R, S, Q, NQ (**inertial**)
R <= '0', '1' after 25 ns, '0' after 30 ns;
S <= '1', '0' after 20 ns, '1' after 35 ns, '0' after 50 ns;
 - (c) Write entity-architecture for a transport model
 - (d) Given the waveform in (b) draw, R, S, Q, NQ (**transport**)

Assignment #2 (Part 2 of 3)

 

(2) Given the above two tri-state buffers connected together (assume transport model of 5ns per gate), draw **X**, **Y**, **F**, **a**, **b**, **G** for the following input waveforms:

X <= '1', '0' after 10 ns, '1' after 20 ns, 'L' after 30 ns, '1' after 40 ns;


Y <= '0', 'L' after 10 ns, 'W' after 20 ns, 'Z' after 30 ns, 0 after 40 ns;

F <= '0', '1' after 10 ns, '0' after 50 ns;

Assignment #2 (Part 3 of 3)

3a) Write **(no programming)** a entity-architecture for a **1-bit** ALU. The input will consist of **x, y, Cin, f** and the output will be **S** and **Cout**. Use as many sub-components as possible. The input function **f** will enable the following operations:

<u>function f</u>	<u>ALU bit operation</u>
000	$S = 0$ $C_{out} = 0$
001	$S = x$
010	$S = y$
011	$S = x \text{ AND } y$
100	$S = x \text{ OR } y$
101	$S = x \text{ XOR } y$
110	$(C_{out}, S) = x + y + C_{in};$
111	$(C_{out}, S) = \text{full subtractor}$

 

3b) Calculate the number of transistors for the 1-bit ALU

3c) Write a entity-architecture for a N-bit ALU (for-generate)