



EECS 318 CAD Computer Aided Design


LECTURE 5: AOIs, WITH-SELECT-WHEN, WHEN-ELSE

*Instructor: Francis G. Wolff
wolff@eecs.cwru.edu*

Case Western Reserve University



This presentation uses powerpoint animation: please viewshow

DeMorgan's laws: review


 


General Rule:

 
 
1. Exchange the AND with OR
2. Invert the NOTs


  
$$\overline{X Y} = \overline{\overline{X} + \overline{Y}}$$



  
$$\overline{X + Y} = \overline{X} \overline{Y}$$







$$X + Y = \overline{\overline{X} \overline{Y}}$$

CMOS logic gate: review




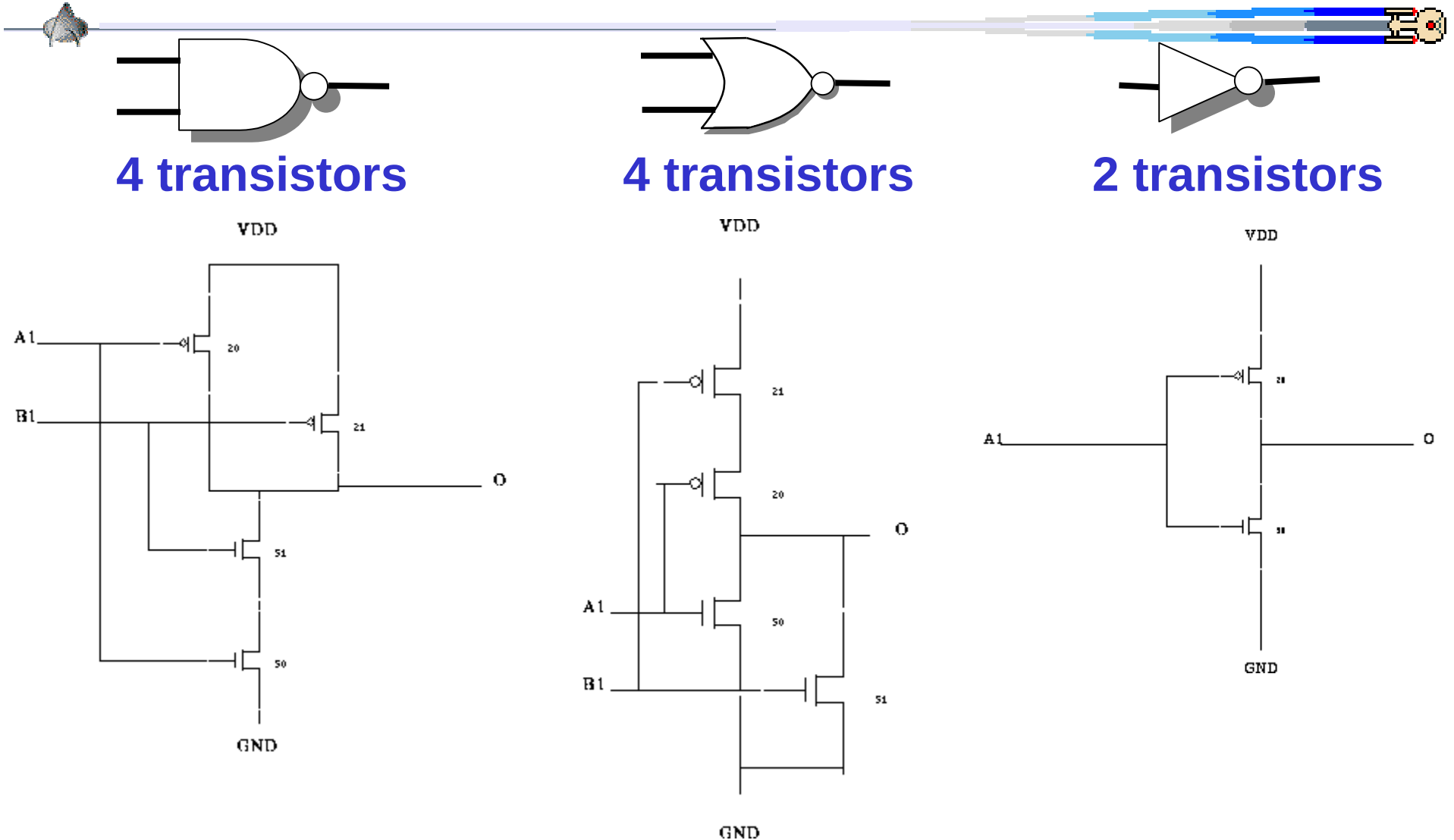


    CMOS logic gate: layout sizes (1X output drive)





AOI: AND-OR-Invert gates

    - Suppose you want to transform a circuit to all nands & nots



AOI: AND-OR-Invert gates

  - Although, there were no tricks to make AND gates better
- AOIs provide a way at the gate level to use **less** transistors than separate ANDs and a NORs
- ASIC design logic builds upon a **standard logic cell library**, therefore, do not optimize transistors **only logic gates**
- For example, 2-wide 2-input AOI will only use **8 transistors**






- Whereas 2 ANDs (12 transistors) and 1 NOR (4 transistors) will use a total of **16 transistors** {14 by DeMorgans law}








AOI: AND-OR-Invert cmos 2x2 example

- For example, 2-wide 2-input AOI (2x2 AOI)

   $O \leq \text{NOT}((D1 \text{ AND } C1) \text{ NOR } (B1 \text{ AND } A1));$




AOI: AND-OR-Invert cmos 2x2 example

       


- This means AOIs use less chip area, less power, and delay

AOI: other Standard Cell examples

 


AOI22 Cell: 2x2 AOI (8 transistors)

 $Y \leq (A \text{ AND } B) \text{ NOR } (C \text{ AND } D);$



AOI23 Cell: 2x3 AOI (10 transistors)

 $Y \leq (A \text{ AND } B) \text{ NOR } (C \text{ AND } D \text{ AND } E);$





AOI21 Cell: 2x1 AOI (6 transistors)

$Y \leq (A \text{ AND } B) \text{ NOR } C;$

Total transistors = 2 times # inputs

AOI: XOR implementation

 
 


The XOR is not as easy as it appears

$Y \leq (A \text{ AND NOT } B) \text{ OR } (\text{NOT } B \text{ AND } A);$

This design uses 22 transistors


$Y \leq \text{NOT}(A \text{ XNOR } B);$

 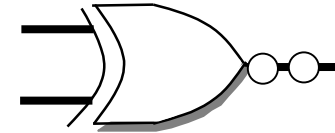

$Y \leq \text{NOT}((A \text{ AND } B) \text{ OR } (\text{NOT } B \text{ AND NOT } A));$

This newer design uses 18 transistors

 But wait, we can exploit the AOI22 structure
now we have $4+4+2+2=12$ transistors






$Y \leq \text{NOT}((A \text{ AND } B) \text{ OR } (B \text{ NOR } A));$

Finally, by applying DeMorgan's law


The total of transistors is now 10

OAI: Or-And-Invert

- Or-And-Inverts are dual of the AOIs

   


with-select-when: 2-to-1 Multiplexor

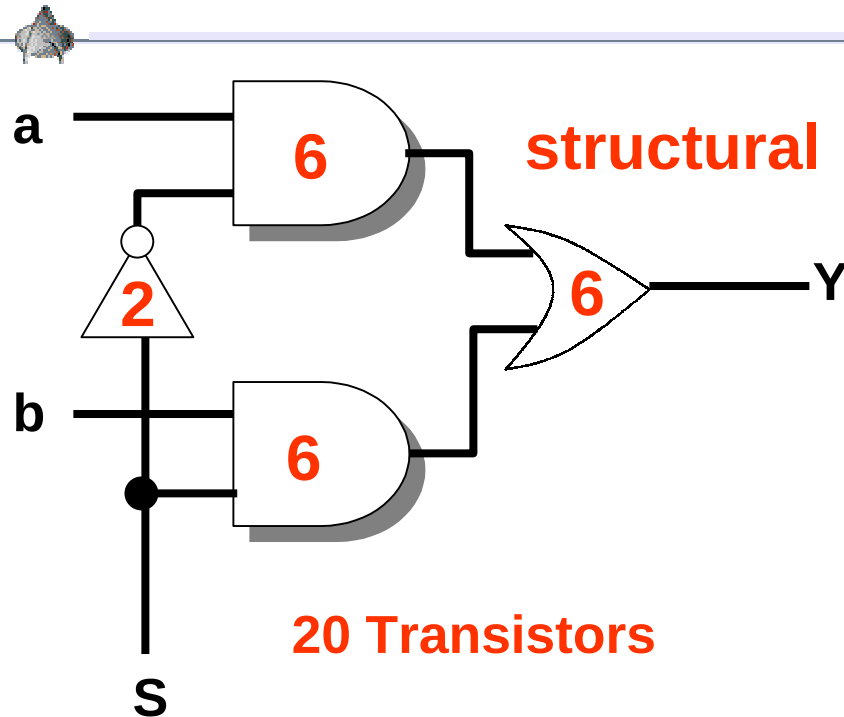

```
Y <= (a AND NOT s)
      OR
      (b AND s);
```

combinatorial logic

 


```
WITH s SELECT
  Y <= a WHEN '0',
      b WHEN '1';
```

or alternatively

```
WITH s SELECT
  Y <= a WHEN '0',
      b WHEN OTHERS;
```


with-select-when: 2 to 4-line Decoder

 

32 Transistors

Replace this
with a NOR,
then 26 total
transistors

 
```
SIGNAL S: std_logic_vector(1 downto 0);  
SIGNAL Y: std_logic_vector(3 downto 0);
```



WITH **S** SELECT

```
Y <= "1000" WHEN "11",  
     "0100" WHEN "10",  
     "0010" WHEN "01",  
     "0001" WHEN OTHERS;
```

ROM: 4 byte Read Only Memory

 

ROM: 4 byte Read Only Memory

```
ENTITY rom_4x8 IS
    PORT(A:    IN std_logic_vector(1 downto 0);
         OE:    IN std_logic; -- Tri-State Output
         D:     OUT std_logic_vector(7 downto 0)
    ); END;
```

```
ARCHITECTURE rom_4x8_arch OF rom_4x8 IS
    SIGNAL ROMout: std_logic_vector(7 downto 0);
BEGIN
    BufferOut: TriStateBuffer GENERIC MAP(8)
        PORT MAP(D, ROMout, OE);

    WITH A SELECT
        ROMout <= "01000001" WHEN "00",
                  "11111011" WHEN "01",
                  "00000110" WHEN "10",
                  "00000000" WHEN "11";
```

when-else: 2-to-1 Multiplexor



WITH **s** SELECT

Y <= **a** WHEN '0',
b WHEN '1';


Y <= **a** WHEN **s** = '0' ELSE
b WHEN **s** = '1';

or alternatively

WITH **s** SELECT

Y <= **a** WHEN '0',
b WHEN OTHERS;


Y <= **a** WHEN **s** = '0' ELSE
b;

 

WHEN-ELSE condition
allows a condition as part
of the WHEN

whereas the WITH-SELECT
only allows only a value as
part of the WHEN.

with-select-when: 4-to-1 Multiplexor

 


As long as each WHEN-ELSE condition is **mutually exclusive**, then it is equivalent to the WITH-SELECT statement.

WITH s SELECT

```
Y <= a WHEN "00",  
      b WHEN "01",  
      c WHEN "10",  
      d WHEN OTHERS;
```

```
Y <= a WHEN s = "00" ELSE  
      b WHEN s = "01" ELSE  
      c WHEN s = "10" ELSE  
      d ;
```

when-else: 2-level priority selector

 

```
Y <= a WHEN s(1) = '1'  
ELSE  
    b WHEN s(0) = '1'  
ELSE  
    '0';
```


WHEN-ELSE are useful for sequential or **priority encoders**

WITH-SELECT-WHEN are useful for parallel or **multiplexors**

WITH **s** SELECT

```
Y <= a WHEN "11",  
    a WHEN "10",  
    b WHEN "01",  
    '0' WHEN OTHERS;
```

when-else: 3-level priority selector

 

WITH *s* SELECT


Y <= *a* WHEN "111",
a WHEN "110",
a WHEN "101",
a WHEN "100",
b WHEN "011",
b WHEN "010",
c WHEN "001",
'0' WHEN OTHERS;

Y <= *a* WHEN *s*(2) = '1' ELSE
b WHEN *s*(1) = '1' ELSE
c WHEN *s*(0) = '1' ELSE
'0';

when-else: 2-Bit Priority Encoder (~74LS148)




 - Priority encoders are typically used as interrupt controllers
- The example below is based on the 74LS148



I_3	I_2	I_1	I_0	G_S	A_1	A_0
0	X	X	X	0	0	0
1	0	X	X	0	0	1
1	1	0	X	0	1	0
1	1	1	0	0	1	1
1	1	1	1	1	1	1

 when-else: 2-Bit Priority Encoder (~74LS148)




```
ENTITY PriEn2 IS PORT(  
  I:    IN    std_logic_vector(3 downto 0);  
  GS:   OUT std_logic;  
  A:    OUT std_logic_vector(1 downto 0);  
); END;
```

I_3	I_2	I_1	I_0	G_S	A_1	A_0
0	X	X	X	0	0	0
1	0	X	X	0	0	1
1	1	0	X	0	1	0
1	1	1	0	0	1	1
1	1	1	1	1	1	1

```
A <= "00" WHEN  $I_3$  = 0 ELSE  
      "01" WHEN  $I_2$  = 0 ELSE  
      "10" WHEN  $I_1$  = 0 ELSE  
      "11" WHEN  $I_0$  = 0 ELSE  
      "11" WHEN OTHERS;
```

 when-else: 2-Bit Priority Encoder (~74LS148)



Structural model

```
GS <= NOT( NOT(I3) OR NOT(I2)
           OR NOT(I1) OR NOT(I0) )
```

I ₃	I ₂	I ₁	I ₀	G _s	A ₁	A ₀
0	X	X	X	0	0	0
1	0	X	X	0	0	1
1	1	0	X	0	1	0
1	1	1	0	0	1	1
1	1	1	1	1	1	1

Structural model

```
GS <= I3 AND I2 AND I1 AND I0
```

Behavioral model

```
GS <= WITH I SELECT
      '1' WHEN "1111",
      '0' WHEN OTHERS;
```